

Larbi Ben Mhidi University of Oum El Boaghi
Faculty of Exact Sciences and Natural and Life Sciences
Department of Material Sciences
2 YL Physics (S3), 2024-2025

PW N° 1 : Measurement of Currents and Voltages

Objectives :

- Use a voltmeter and ammeter correctly.
- Properly wiring an electrical circuit.
- Interpret the results found.

Evaluation criteria :

- Correct wiring.
- The student's working method.
- Accuracy of results.

Material used :

- Resistance.
- Voltage generator.
- Voltmeter, ammeter and multimeter.

Reminder :

1) The electrical voltage:

It is a potential difference (d.d.p) between two points, which reflects an electrical imbalance or different electric charges, it is measured by a voltmeter.

The voltmeter is a device that connects in parallel with the component or dipole whose voltage is to be measured at its terminals. There are two types of voltmeters:

- The analog voltmeter (needle or deflection).
- The voltmeter with digital display.

The insertion of a voltmeter into a circuit generates errors in the measurement, in fact, when subjected to a voltage U_v , the voltmeter of resistance R_v consumes a current I_v such that :

$$I_v = \frac{U_v}{R_v}$$

To decrease the error, we must decrease the current I_v and consequently increase the resistance R_v . In summary, a voltmeter must have a very high resistance R_v in relation to the internal resistance of the dipole whose voltage is to be measured.

Remarks:

- A perfect voltmeter admits an infinite R_v resistance.
- To determine the resistance R_v of each caliber of an analog voltmeter, the manufacturer provides us with the specific resistance S of each device indicated in the middle of the dial expressed in Ohm per volt (Ω/V).

Example: for $C = 30V$, $S = 20000 \rightarrow R_v = 20000 \times 30 = 60K\Omega$.

2) Electric current :

Electric current results from the movement of electrical charges between two points in a branch. Its intensity reflects the flow rate of the moving charges, it is measured by an ammeter.

The ammeter is a device that is connected in series with the component(s) through which the current is to be measured. There are two types of ammeters :

- The analog ammeter (needle or deflection).
- The digital display ammeter.

The insertion of an ammeter in a circuit generates errors in the measurement in fact, crossed by a current I , the R_A resistance ammeter causes a drop in voltage U_A in the circuit such that :

$$U_A = R_A \cdot I$$

To decrease the error, we must decrease the U_A voltage and consequently decrease the R_A resistance. In summary, an ammeter must have a very small R_A resistance compared to the sum of the internal resistances of the dipoles traversed by the same current to be measured.

Note : A perfect ammeter admits an R_A resistance of zero.

3) Evaluation of a measure :

In the case of a digital device: whether it is a voltmeter or a digital ammeter, the measurement is read directly on the dial of the device, to be accurate you just have to choose the right caliber.

In the case of an analog device: using this type of device the measurement is not direct, to determine it, the following relationship must be applied :

$$Size = \frac{Caliber \times Reading}{Scale}$$

with:

- Quantity: the quantity to be measured (voltage U or current I).
- Caliber: denoted C , this is the caliber used.
- Reading: denoted L , this is the deflection of the needle.
- Scale: denoted E , this is the scale used that corresponds to the maximum deviation.

4) Error Assessment :

Other than the error caused by the insertion of a device into a circuit, there are other errors that cannot be avoided, namely errors caused by the device itself and errors made by the operator.

- In the case of digital cameras: to assess the absolute uncertainty, reference must be made to the technical instructions of the device, the manufacturer mentions for each calibre (range) the relationship that must be applied. The general form of these relations is as follows :

$$\Delta G_{\text{Measure}} = X\% (\text{Reading}) + Y\% \text{ of points } (\text{Range})$$

$$\Delta G_{\text{measure}} = \frac{\text{Measured value} \cdot X}{100} + \frac{\text{Range} \cdot Y}{\text{Total Points}}$$

- In the case of analogue devices: the absolute uncertainty is the sum of the class uncertainty and the reading uncertainty.

$$\Delta G_{\text{Measure}} = \Delta G_{\text{Class}} + \Delta G_{\text{Reading}}$$


$$\Delta G_{\text{Class}} = \frac{\text{Class} \cdot \text{Caliber}}{100}, \quad \Delta G_{\text{Reading}} = \frac{\text{Caliber} \cdot \text{Estimated number of graduations}}{\text{Scale}}$$

with:

- Class: denoted Cl, this is the class of the device indicated on the dial.
- Number of ticks: denoted n, this is the number of ticks estimated as an error value.

Manipulation :

On considère le circuit suivant :

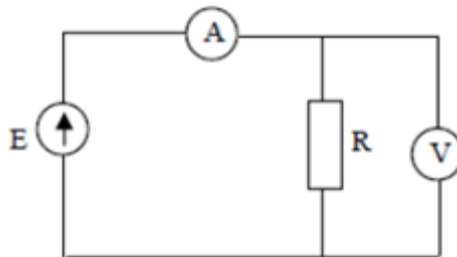

1) Assemble the previous circuit (the values of the resistors and emfs are set by the teacher).

2) Complete the following tables:

E (V)	R (Ω)	I (mA)	U(V)
5	1000		
8	1500		
11	2000		
15	2500		
20	3000		