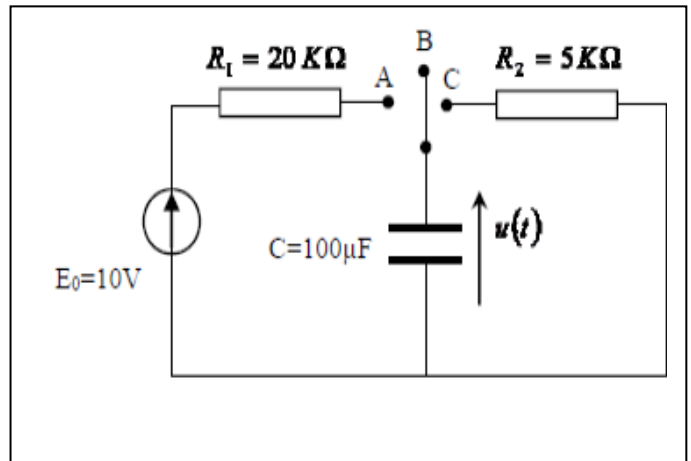


Tutorial 2

Exercise 1:

In the circuit shown in the following figure, the switch is initially located in the position B and the capacitor is discharged. At time $t = 0$, we toggle the in position A. After 10 seconds, it is switches to position C.

- Plot the evolution of the voltage $u(t)$.



Correction 1:


1) The switch in position A :

The assembly becomes as follows :

Law of meshes : $E = U_{R1} + U(t) = R_1 C \cdot dU(t)/dt + U(t)$
Is a 1st order differential equation with the solution :


$U(t) = E(1 - \exp(-t/\tau))$,
with $\tau = 2 \cdot 10^4 \cdot 10^{-4} = 2s$, and $E = 10 V$.

Therefore, $U(t) = 10(1 - \exp(-t/2))$

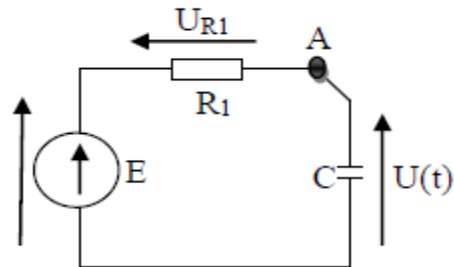

t	0	0.5	1	2	2.5	3	4	5	6	7	8	9	10
U(t)	0	2.2	3.8	5.2	6.3	7.2	8.7	9.2	9.5	9.7	9.8	9.8	9.9

Graph of $U(t)$:

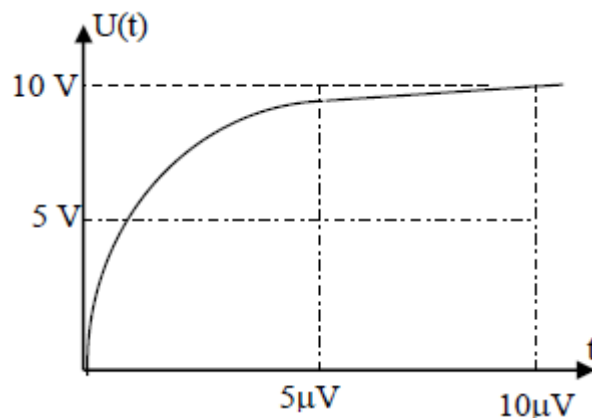


2) The switch in position C:

The assembly becomes as follows :

Law of meshes : $U_{R2} + U(t) = R_2 C \cdot dU(t)/dt + U(t) = 0$
is a 1st order differential equation with the solution :

$U(t) = E \exp(-t/\tau)$, $\tau = 5 \cdot 10^3 \cdot 10^{-4} = 0,5 s$, et $E = 10 V$.


$U(t) = 10 \cdot \exp(-2t)$

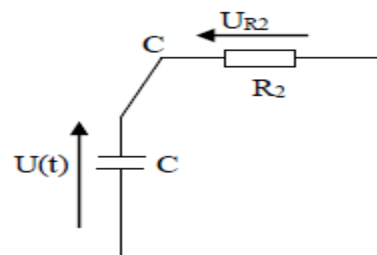

Tutorial 2

The graph of $U(t)$

t	0	0.5	1	2	2.5	3	4	5
$U(t)$	10	3.7	1.3	0.18	0.06	0.02	0.003	0.0004

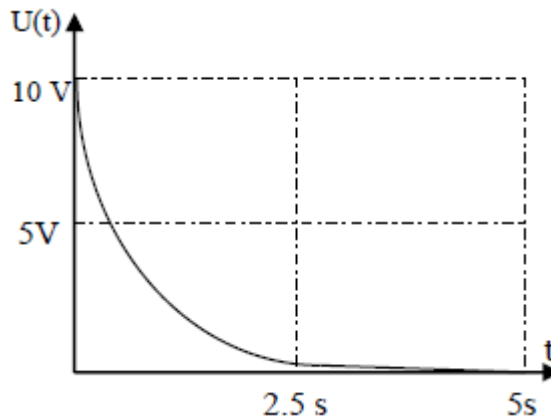

Exercise 2 :

Same set-up and data from the previous year.

- Plot the evolution of the current $i(t)$.

Exercise 3 :

1) Calculate the percentage of charge of a capacitor $C = 100 \mu\text{F}$ charged through a resistor $R = 20 \text{ K}\Omega$ for $t = \tau$.

$E = 10 \text{ V}$.

2) Determine how to increase the charging speed.

Correction 3 :

1) $\tau = R.C = 2.10^4.10^{-4} = 2\text{s}$.

$$U(t = \tau) = U(\tau) = E(1 - \exp(-t/\tau)) = 10(1 - \exp(-1)) = 10 - 10/\exp(1) = 10 - 10/2.72$$

$$U(\tau) = 6.33 \text{ V}.$$

$$10 \text{ V} \quad \rightarrow \quad 100 \%$$

$$6.33 \quad \rightarrow \quad x \%$$

$$x \% = (6.33 \times 100) / 10 = 63.3 \%$$


2) To increase the charging speed, you have to decrease τ ($\tau = RC$).

Exercise 4 :

At $t = 0$ we close the switch:

We give: $R = 6000 \Omega$, $L = 30\text{mH}$, $E = 6\text{V}$.

1. Applying Kirchhoff's Law to Nodes
2. Applying Kirchhoff's Law to the Principal Mesh
3. Find the expression of the generating current.

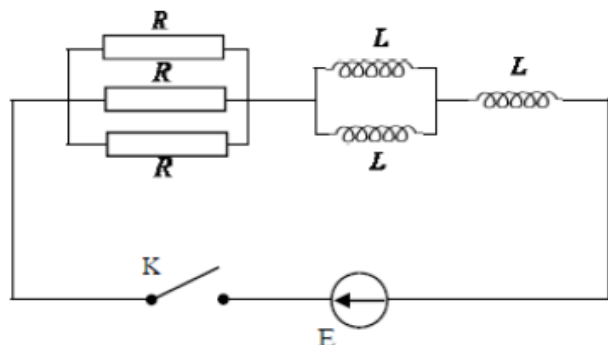

Tutorial 2

Correction 4 :

1. There are 4 nodes (A, B, C, and D):

At point A : $i(t) = I_R + I_R + I_R$, At point B : $I_R + I_R + I_R = i(t)$

At point C : $i(t) = I_L + I_L$, At point D: $I_L + I_L = i(t)$

2. $E = L_{eq}.di/dt + R_{eq}.i(t)$.

$$L_{eq} = L_{eq1} + L = L/2 + L = 3L/2$$

$$R_{eq} = R/3$$

Therefore, $(3L/2).di/dt + (R/3).i(t) = E$ (Differential equation of order 1)

solution : $i(t) = E(1 - \exp(-3t/RL))$.

D.A : $i(t) = 6(1 - \exp(-t/60))$.