

Larbi Ben Mhidi University of Oum El Boaghi
Faculty of Exact Sciences and Natural and Life Sciences
Department of Material Sciences
2 YL Physics (S3), 2024-2025

PW N° 2 : Law of meshes and laws of knots

I) Voltage measurement and voltage laws:

The electrical state of a point X is characterized by its electric potential denoted V_X . It is measured in volts (V). An electrical voltage between two points reflects a difference in electrical states between these two points: The U_{XY} voltage between the X and Y points of a circuit is $U_{XY} = V_X - V_Y$.

Reminder: A voltmeter plugs into to measure the voltage between 2 points X and Y of an electrical circuit denoted U_{XY} . The V terminal of the voltmeter is connected to point X and the COM terminal to point Y.

Carry out the assembly 1.

With $R_1 = 1000 \Omega$

$R_2 = 470 \Omega$ and a switch

A DC generator set to 6 V.

Measure successively:

• $U_{PN} = \dots\dots\dots$, $U_{NP} = \dots\dots\dots$

1st conclusion: Tension is a quantity

• $U_{AB} = \dots\dots\dots$, $U_{BC} = \dots\dots\dots$, $U_{AC} = \dots\dots\dots$


2nd conclusion: Law's.....:

.....

• $U_{PA} = \dots\dots\dots$ $U_{CN} = \dots\dots\dots \approx \dots\dots\dots V$

3rd conclusion: The voltage across a wire is

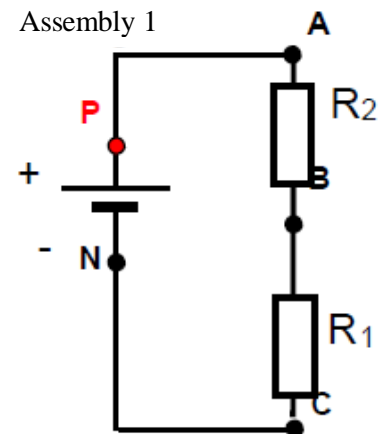• Calculate $U_{NP} + U_{PA} + U_{AB} + U_{BC} + U_{CN} = \dots\dots\dots$: This is the law of meshes.



II) Measurement of intensities and associated law

The intensity of the current is defined as the electric charge carried by electrons passing through a section of circuit for one second. It is measured in amperes denoted A. It is an algebraic quantity.

Reminder: Outside a generator, the current flows from the pole to the pole An ammeter is connected to: To make the measurement, a wire must be removed from the circuit. The A (or mA) and COM terminals are used. The value indicated by the ammeter is positive if the current actually enters through the A terminal (or mA) and exits through the COM terminal (negative otherwise).

Carry out the assembly 2.

with: $R_1 = 1000 \, \Omega$

$R_2 = 470 \, \Omega$

a switch

a DC generator set to 6 V.

If you don't make a mistake, the intensities to be measured will be less than 100 mA; We will therefore be able to use the inputs mA and COM of the ammeter.

Measure the currents of the I-rated currents in the branch

I_1 and I_2 :

• $I = \dots\dots\dots I_1 = \dots\dots\dots I_2 = \dots\dots\dots$

Conclusion: law of

