

If a sinusoidal voltage (or current) is imposed on a network, a sinusoidal response of the same frequency as the applied voltage (or current) appears, in addition to the transient regime. When the transient regime has disappeared, this sinusoidal response remains: it is the permanent sinusoidal regime. In this part, we study linear circuits in which the signals imposed by the generators are sinusoidal.

1. Sinusoidal quantities

A signal is said to be sinusoidal if it is of the form : $X(t) = X_m \cos(\omega t + \varphi) = X\sqrt{2}\cos(\omega t + \varphi)$

X_m : Amplitude of the signal.


ω : pulsation of the periodic signal and is expressed in (rad/s).

$T = \frac{2\pi}{\omega}$: Signal period, $f = \frac{1}{T} = \frac{\omega}{2\pi}$: Signal frequency.

$\omega t + \varphi$: is the phase of the signal and is expressed in radians (rad).

φ : Initial phase of the signal (at $t = 0$).

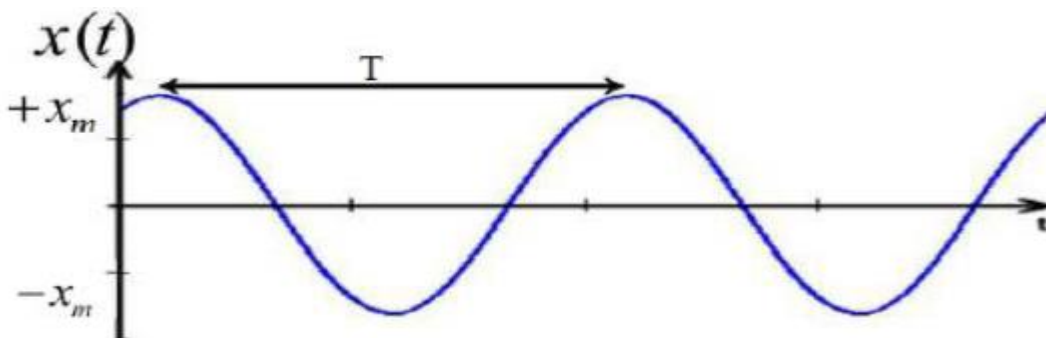X : Effective value defined by : $X^2 = \frac{1}{T} \int_0^T x^2(t) dt$, we obtain $X = \frac{x_m}{\sqrt{2}}$



2. Representations of sinusoidal quantities

2.1. Vector representation (Fresnel method)


This method allows the addition of instantaneous sinusoidal quantities of the same frequency, but of different amplitudes and phases.

- Consider two sinusoidal currents :

$$i_1(t) = I_{m1} \cos(\omega t + \varphi_1) \quad \text{and} \quad i_2(t) = I_{m2} \cos(\omega t + \varphi_1)$$

The sum of the two currents is : $i(t) = i_1(t) + i_2(t)$.

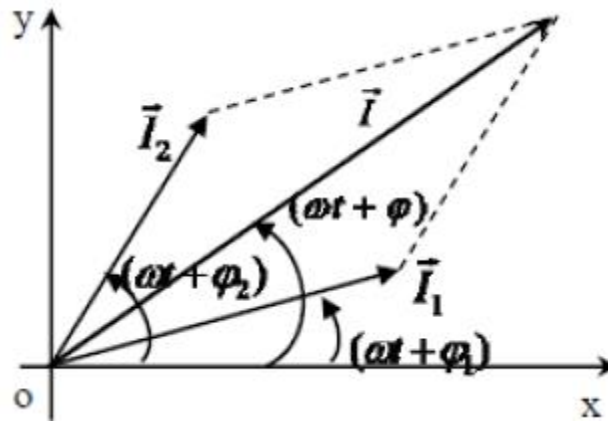- To find $i(t)$, we can proceed graphically :



- Consider a vector denoted \vec{I}_1 of I_{m1} standard, rotating in the plane xOy at an angular velocity ω , and whose angle with the Ox axis at a time t is equal to $\omega t + \varphi_1$. We define a vector in the same way \vec{I}_2
- The projections on Ox of the vectors \vec{I}_1 and \vec{I}_2 are equal to the currents i_1 and i_2 respectively.

The sum of the two currents $i(t)$ is the projection of the sum vector :

$$i(t) = I_m \cos(\omega t + \varphi) \text{ et } \vec{I} = \vec{I}_1 + \vec{I}_2, \text{ such as } \|\vec{I}\| = I_m$$

2.2. Complex representation


2.2.1. Mathematical reminders

- A complex number can be put in the form: $Z = a + jb$

We call: $a = R(Z)$ the real part.

and $b = \text{Im}(Z)$ the imaginary part.

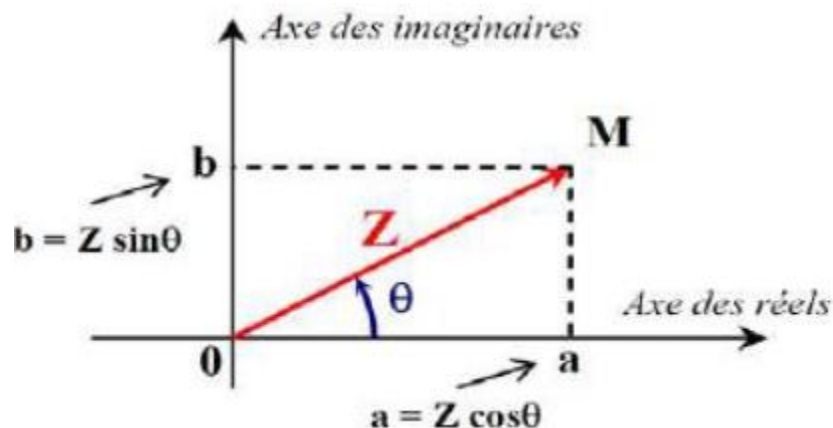- We can associate a vector \vec{OM} in the complex plane: $Z = r \cos \theta + j r \sin \theta$



$r = |Z| = \sqrt{a^2 + b^2}$: modulus of the complex number

$\theta = \arg(Z) = \arctan \frac{b}{a}$: argument (angle) of the complex number

- It can also be written in the exponential form: $Z = re^{j\theta}$
- or in polar form: $Z = [r, \theta] = r \angle \theta$
- special case: $J = e^{j\frac{\pi}{2}}$

2.2.2. Application to sinusoidal signals

A sinusoidal signal $x(t)$ is associated with a complex time quantity \underline{X} :

$$x(t) = x_m \cos(\omega t + \varphi) = R(\underline{X}e^{j\omega t}), \quad \underline{X} = x_m e^{j\varphi} = X\sqrt{2} \cdot e^{j\varphi}$$

$$x(t) \Leftrightarrow \underline{X}$$

X_m : modulus of the complex quantity ($|\underline{X}|$),

φ : argument of the complex quantity ($\arg \underline{X}$),

$X = X_m/\sqrt{2}$: effective value.

Note : We will note $x(t)$ as the instantaneous value, X as the RMS value, and \underline{X} as the complex value.

2.2.3. Derivative and integration

Let the function $x(t) = x_m \cos(\omega t + \varphi)$, the derivative is written :

$$\frac{dx}{dt} = -x_m \omega \sin(\omega t + \varphi) = x_m \cos\left(\omega t + \varphi + \frac{\pi}{2}\right)$$

It is associated with the complex amplitude :

$$\omega x_m e^{j(\omega t + \varphi + \frac{\pi}{2})} = j\omega x_m e^{j(\omega t + \varphi)} = j\omega \underline{X} e^{j\omega t}$$

Therefore : $\frac{dx}{dt} = j\omega \underline{X}$

In the same way, it is shown that the integral is equivalent to dividing by $j\omega$: $\int x dx = \frac{1}{j\omega} \underline{X}$

3. Complex model of a circuit in the sinusoidal regime

In a sinusoidal circuit, we can write :

$$e(t) = E_0 \cos \omega t = R(\underline{E} e^{j\omega t}), \quad \underline{E} = E_0$$

The voltage source $e(t)$ is replaced by its complex form denoted \underline{E} :


$$e(t) \Leftrightarrow \underline{E} = E_0$$

In the complex model, any linear dipole has a complex impedance : $Z = R + jX$
 where R : represents the resistance of the dipole.

X : reactance.

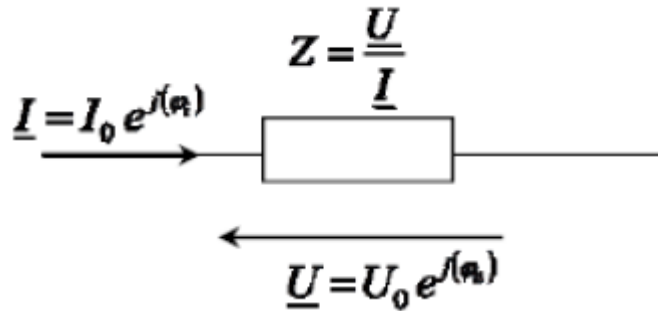3.1. Complex impedances of elementary dipoles

The complex impedance Z is defined for a linear dipole as being equal to the ratio of the value complex of the voltage \underline{U} on the complex value of the current \underline{I} : $Z = \frac{\underline{U}}{\underline{I}}$



3.1.1. Impedance of a resistor

we have: $u(t) = R i(t)$

Moving on to the complex amplitudes, we then obtain: $\underline{U} = \underline{Z} \cdot \underline{I}$

In the case of a resistor, the complex impedance is equal to R : $\underline{Z}_R = R$.

3.1.2. Impedance of an ideal coil

The relationship between current and voltage across an inductor coil L is: $u(t) = L \frac{di(t)}{dt}$

This temporal relationship is expressed in terms of complex amplitudes by : $\underline{U} = jL\omega \underline{I}$

The definition of the complex impedance of a linear dipole then allows us to set $\underline{Z}_L = jL\omega$

3.1.3. Impedance of a capacitor

The relationship between current and voltage across an ideal capacitor of capacitance C is

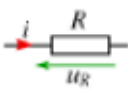
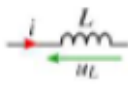
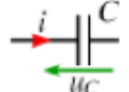
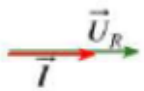

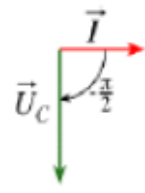
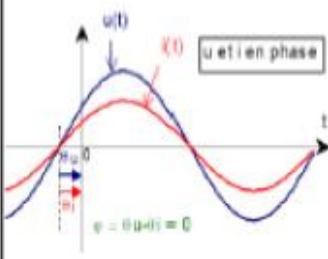
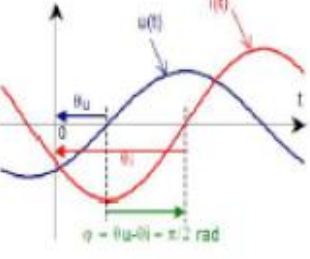
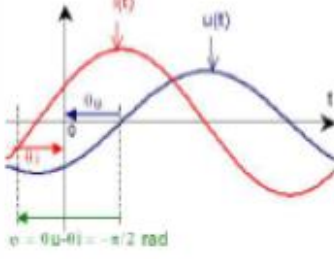
$U(t) = \frac{1}{C} \int i(t) dt$. We deduct $\underline{U} = \frac{1}{jC\omega} \underline{I}$

The expression of the capacitor impedance is written: $\underline{Z}_C = \frac{1}{jC\omega}$

3.2. Sinusoidal Laws

All laws seen in a continuous regime are applicable to sinusoidal regimes provided that they are Apply to snapshot values or complex values.

Chap 3 : Sinusoidal power grids

	Résistance R	Inductance L	Capacité C
Schéma			
Equation fondamentale	$u_R(t) = R i(t)$	$u_L(t) = L \frac{di(t)}{dt}$	$u_C(t) = \frac{1}{C} \int i(t) dt$
Equation complexe	$\underline{U}_R = R \underline{I}$	$\underline{U}_L = jL\omega \underline{I}$	$\underline{U}_C = \frac{1}{jC\omega} \underline{I}$
Impédance Z (Ω)	$Z_R = R$	$Z_L = jL\omega$	$Z_C = \frac{-j}{C\omega}$
Admittance Y (S)	$Y_R = \frac{1}{R}$	$Y_L = -\frac{j}{L\omega}$	$Y_C = jC\omega$
Déphasage $\varphi(\text{rad}) = \Delta\varphi = \varphi_u - \varphi_i$	$\varphi_R = 0$	$\varphi_L = \frac{\pi}{2}$	$\varphi_C = -\frac{\pi}{2}$
Représentation de Fresnel	 Le courant est en phase avec la tension	 Le courant est en retard de $\pi/2$ sur la tension	 Le courant est en avance de $\pi/2$ sur la tension
Relations de phase	 $\varphi = \theta_u - \theta_i = 0$	 $\varphi = \theta_u - \theta_i = \pi/2 \text{ rad}$	 $\varphi = \theta_u - \theta_i = -\pi/2 \text{ rad}$

3.3. Passive Dipole Grouping

Let be a grouping of passive dipoles, with complex impedance Z_i and complex admittance $Y_i = 1/Z_i$.


The equivalent impedance is :

Series association



$$\underline{Z} = \sum_{i=1}^n \underline{Z}_i$$


Parallel association

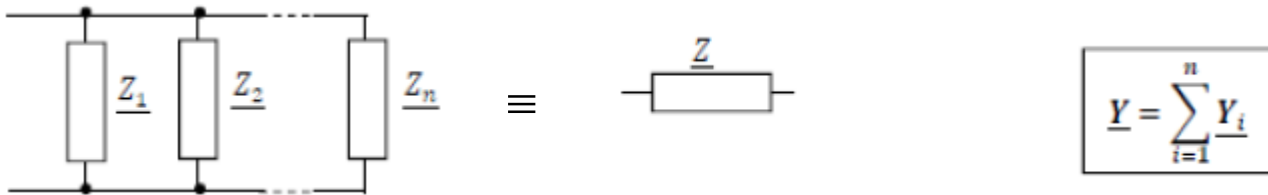

What was true for the association of resistors remains applicable to the association of impedances.

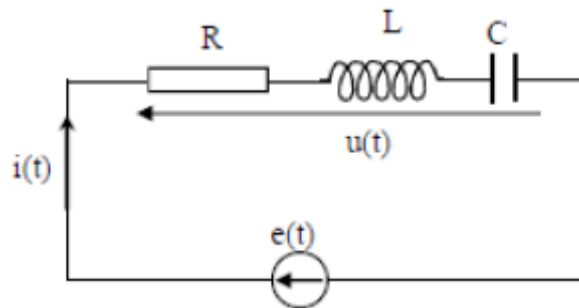3.3. Study of a serial RLC circuit

A sinusoidal generator delivering a voltage $e(t)$, an ohmic conductor of resistor R , a perfect coil of inductance L and a capacitor of capacitance C .



With: $e(t) = E\sqrt{2}\cos\omega t$ and $i(t) = I\sqrt{2}\cos\omega t$

$$U_R = Ri(t), U_L = L \frac{di(t)}{dt} \text{ et } U_C = \frac{1}{C} \int i dt$$

Loi des mailles : $U(t) = U_R + U_L + U_C = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i dt = e$

$$e = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int i dt$$

We replace $i(t)$ and $e(t)$ with their complex notation :

$$\underline{E} = R\underline{I} + jL\omega\underline{I} + \frac{1}{jC\omega}\underline{I} = (R + j(L\omega - \frac{1}{C\omega}))\underline{I}, \text{ So, we have : } \underline{U} = \underline{Z}\underline{I}$$

We find the impedance: $\underline{Z} = R + j(L\omega - 1/C\omega)$, and its modulus : $|\underline{Z}| = \sqrt{R^2 + (L\omega - 1/C\omega)^2}$

And the argument: $\varphi = \arctan \frac{(L\omega - \frac{1}{C\omega})}{R}$


Resonance in intensity

In a series RLC circuit, when the generator imposes a pulsation $\omega = \omega_0$ (the proper pulsation), the circuit enters into intensity resonance, the intensity of the current is then maximum :

$$\underline{I} = \frac{\underline{E}}{\underline{Z}} = \frac{\underline{E}}{R + j(L\omega - \frac{1}{C\omega})}$$

I is maximum, when the denominator is minimal : $L\omega - (1/C\omega) = 0$. So we will have :

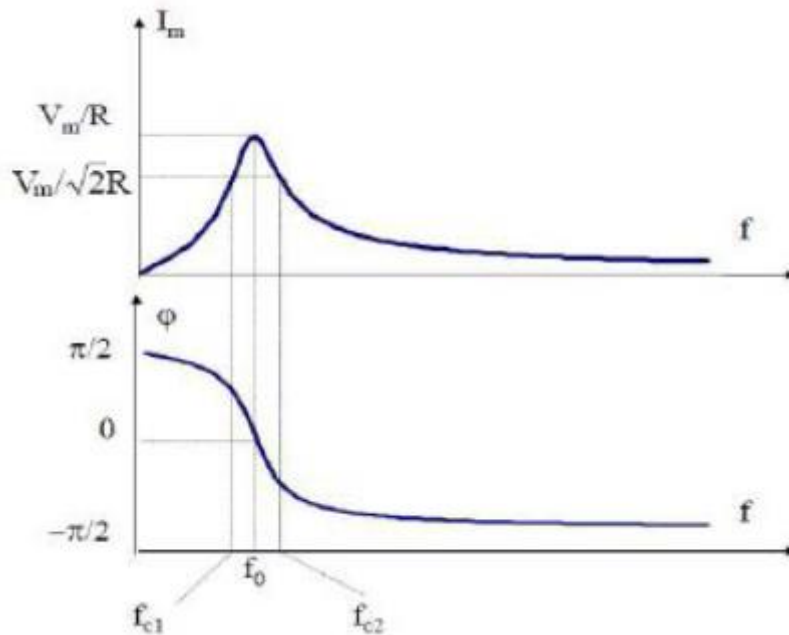- Proper pulse ω_0 : $LC\omega_0^2 = 1, \omega_0 = \frac{1}{\sqrt{LC}}$
- Natural frequency f_0 : $f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$
- The impedance of the circuit is minimal and real: $Z = R$
- The phase shift is zero: $\varphi = 0$



- Bandwidth: $\Delta\omega = \omega_2 - \omega_1$, ω_1 and ω_2 are values of ω for which $I = I_m/\sqrt{2}$

The width of this bandwidth is: $\Delta\omega = \omega_2 - \omega_1 = \omega_0/Q$

- The resonance acuity is expressed using the quality factor of the circuit Q :

$$Q = \frac{L\omega_0}{R} = \frac{1}{RC\omega_0} = \frac{1}{R} \sqrt{\frac{L}{C}}, \quad \text{The greater the quality factor, the higher the resonance.}$$

3.5. Puissance

3.5.1. Puissance instantanée

Let us say: $u(t) = U\sqrt{2}\cos(\omega t + \varphi)$ the voltage across a dipole,
 $i(t) = I\sqrt{2}\cos\omega t$ the intensity of the current that passes through it.

The power received by this dipole is defined by: $p(t) = u(t).i(t)$.

$$p(t) = 2U.I \cos(\omega t) \cos(\omega t + \varphi) = UI \cos\varphi + UI \cos(2\omega t + \varphi)$$

It is noted that power is a periodic function of period $T/2$ with respect to $u(t)$ and $i(t)$.

3.5.2. Average power

The average power P is defined by : $p(t) = (1/T) \cdot \int p(t) dt = UI \cos \varphi$

Power is also called active power in sinusoidal regime.

The perfect coil ($\varphi = \pi/2$) and the capacitor ($\varphi = \pi/2$) do not consume active power and therefore no energy.