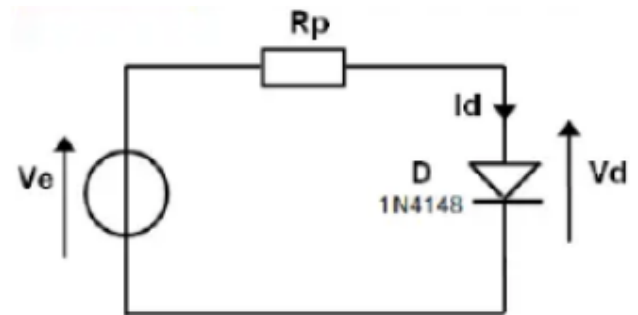


Exercise 1 :

Let us consider the diagram opposite :

We give $V_e = 5 \text{ V}$, $R_p = 1 \text{ K}\Omega$ and $V_s = 0.6 \text{ V}$.

Determine the current value I_d .



Solution 1 :

$$V_e = R_p \cdot I_d + V_s \Rightarrow$$

$$V_e - V_s = R_p \cdot I_d \Rightarrow$$

$$I_d = (V_e - V_s) / R_p = 4,4 / (10^3) = 4,4 \cdot 10^{-3} \text{ A} = 4,4 \text{ mA}$$

Exercise 2 :


Let us consider the diagram opposite:

Knowing that the standard I_f and V_f values

Red LEDs $\phi 5\text{mm}$ are $I_f = 10 \text{ mA}$ and

$V_f = 1.6 \text{ V}$ and $V_e = +5 \text{ V}$.

Determine the value of the resistance R_p allowing the LED to be properly polarized.

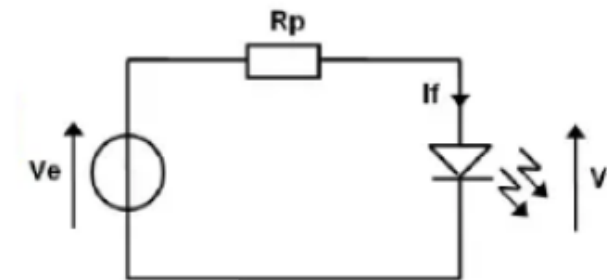

Solution 2 :


$$V_e = R_p \cdot I_f + V_f \Rightarrow V_e - V_f = R_p \cdot I_f \Rightarrow R_p = (V_e - V_f) / I_f = 3,4 / 10^{-2} = 340 \Omega.$$

Exercise 3 :

Let us consider the diagram opposite:

1) Indicate on the diagram, the voltage V_{R1} (at the Terminals of $R1$) and current I (in the direction positive when it exists).

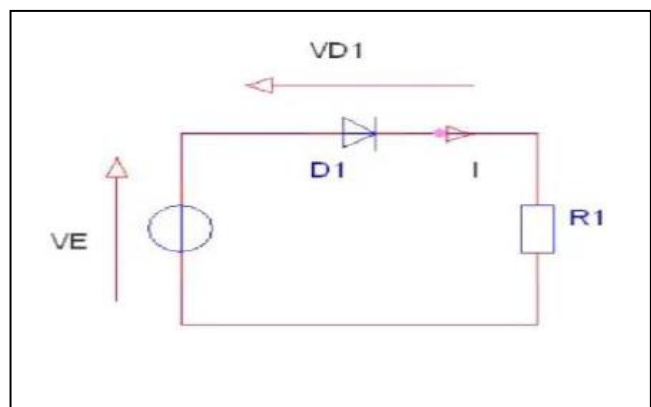2) Knowing that $V_{D1_{\text{threshold}}} = 0.7 \text{ V}$.



What is the value of V_e if the diode is

Blocked.

Solution 3:

1) De bas en haut de R_1 .

2) $V_e = V_{D1} + R_1 I$

D_1 bloquée $\Rightarrow I = 0 \Rightarrow V_e = V_{D1}$.

La diode est bloquée si $V_{D1} < 0,7V$

La diode est passante si $V_e > 0,7V$.