

**Larbi Ben Mhidi University of Oum El Boaghi**  
**Faculty of Exact Sciences and Natural and Life Sciences**  
**Department of Material Sciences**  
**2 YL Physics (S3), 2024-2025**

**PW N° 4 : Superposition theorem**

**1. The purpose of the manipulation**

The goal of this lab is to study circuits with several generators (voltage or current) by considering the influence of each generator independently of the others, which will greatly simplify most of the problems.

**2. Theoretical background 2.1. Superposition theorem**

- a. Statement 1: The voltage between two points in an electrical circuit containing several energy sources (generator) is equal to the algebraic sum of the voltages between these two points when each energy source acts alone.
- b. Statement 2: The current intensity in a branch in an electrical circuit contains several currents (generator) is equal to the algebraic sum of the currents in that branch when each energy source acts alone.

**2.1.1. Principle of superposition**

The current  $I$  in a complete circuit branch (or the voltage  $U$ ) is equal to the algebraic sum of the currents (or voltages) that would be imposed by each of the generators, the others being passivated (or neutralized). So to apply the superposition theorem, it is enough to successively short-circuit each generator.

So in a circuit of  $N$  generators:

- State 1: all generators are passivated except for No. 1 → calculation of  $I_1$ .
- State 2: all generators are passivated except for No. 2 → calculation of  $I_2$ .
- State  $N$ : all generators are passivated except for No.  $N$  → calculation of  $I_N$ .
- Current calculation  $I$ :  $I = \sum I_n$

Same principle with tensions:  $U = \sum U_n$

**Remark:**


To passivate a generator is to consider that it is inoperative:

- ✓ For a voltage generator, it means considering that the voltage across its terminals is zero, i.e. replacing the ideal voltage generator with a short circuit.

✓ For a current generator, it is considered that the current flowed is zero.

**Example:**

Let us consider the circuit below:

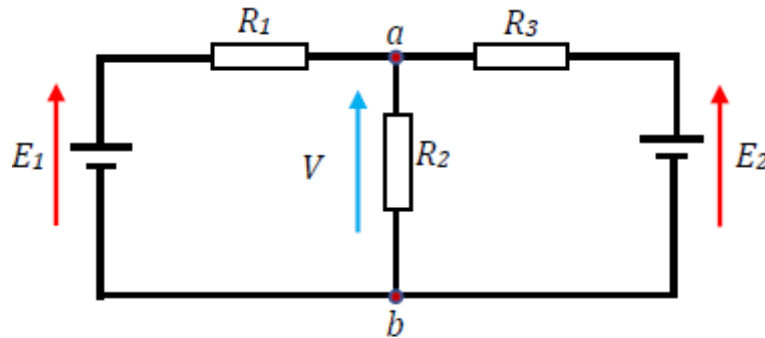

**Figure. 1**

According to the superposition theorem, the voltage  $V$  between the two points  $a$  and  $b$  is:


$$V = V_1 + V_2 \quad (1)$$

With:

- $V_1$  is the voltage between the two points  $a$  and  $b$  when  $E_1$  acts alone (when  $E_2$  is neutralized).
- $V_2$  is the voltage between the two points  $a$  and  $b$  when  $E_2$  acts alone (when  $E_1$  is neutralized).

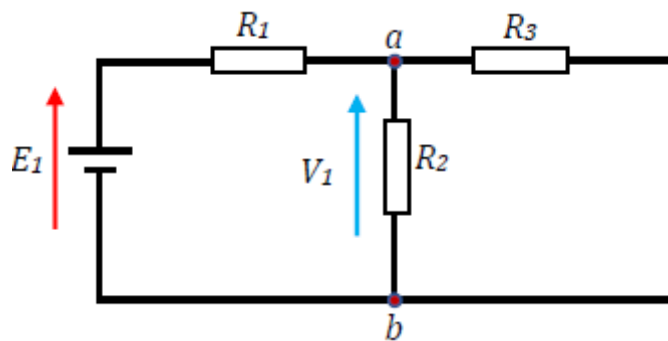**a. Calculate  $V_1$**


By neutralizing  $E_2$  the circuit of the figure. 1 will be as follows:



To calculate the voltage  $V_1$  we must first calculate the equivalent resistance between the two points  $a$  and  $b$  (the equivalent resistance of the two resistors  $R_2$  and  $R_3$  which are in parallel):

$$\frac{1}{R_{eq1}} = \frac{1}{R_2} + \frac{1}{R_3} \quad (2)$$

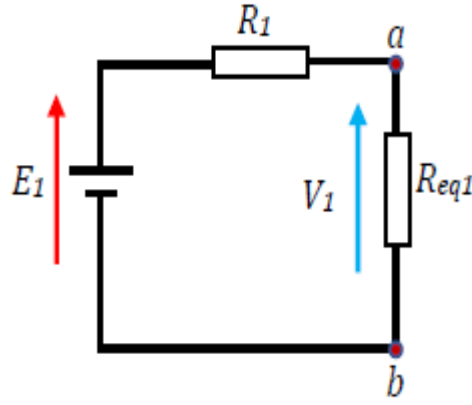So the circuit is reduced to the following:




Using the notion of voltage divider, we find that:

$$V_1 = \frac{R_{eq1}}{R_{eq1} + R_1} E_1 \quad (3)$$
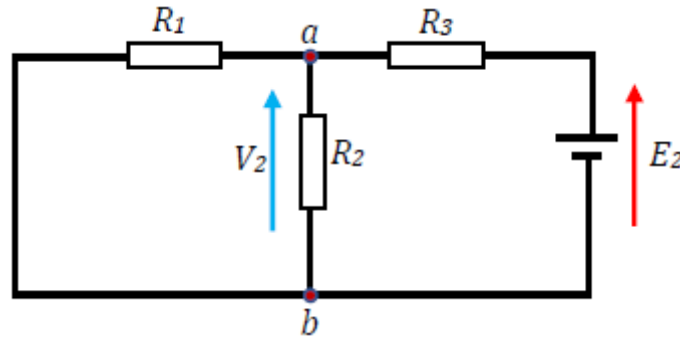
### b. Calculate $V_2$


By neutralizing  $E_1$  the circuit of the figure. 1 will be as follows:



To calculate the voltage  $V_2$ , we must first calculate the equivalent resistance between the two points a and b (the equivalent resistance of the two resistors  $R_1$  and  $R_3$  which are in parallel):

$$\frac{1}{R_{eq2}} = \frac{1}{R_1} + \frac{1}{R_3} \quad (4)$$

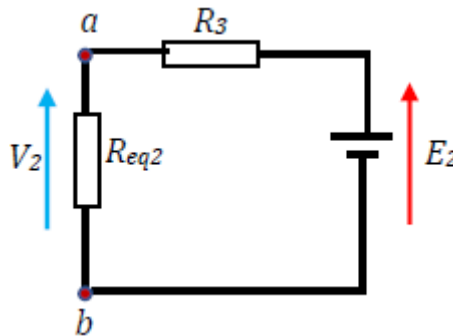So the circuit is reduced to the following:



Using the notion of voltage divider, we find that:

$$V_2 = \frac{R_{eq2}}{R_{eq2} + R_3} E_2 \quad (5)$$


Finally, the voltage  $V$  between the two points a and b is equal to the algebraic sum of the two voltages  $V_1$  and  $V_2$ :

$$V = V_1 + V_2 = \frac{R_{eq1}}{R_{eq1} + R_1} E_1 + \frac{R_{eq2}}{R_{eq2} + R_3} E_2 \quad (6)$$

### 3. Handling

#### 3.1. Implementation

a. Make the following circuit:

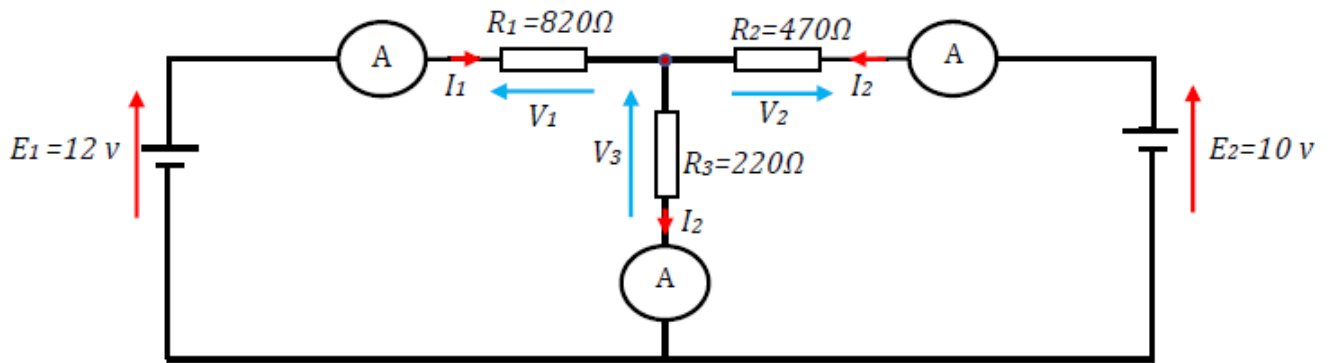

b. Note the different measurements of currents and voltages on the following table:

Tableau. 1

| $V_1$ | $V_2$ | $V_3$ | $I_1$ | $I_2$ | $I_3$ |
|-------|-------|-------|-------|-------|-------|
|       |       |       |       |       |       |

c. Nous allons essayer maintenant de mesurer les courants et les tensions du circuit précédent en utilisant le théorème de superposition.

1. Step 1:  $E_1$  alone,  $E_2$  neutralized:

- Draw and do the Editing?
- Take note of the different measurements of currents and voltages on the following table

Tableau. 2

| $V'_1$ | $V'_2$ | $V'_3$ | $I'_1$ | $I'_2$ | $I'_3$ |
|--------|--------|--------|--------|--------|--------|
|        |        |        |        |        |        |

2. Step 2:  $E_2$  alone,  $E_1$  neutralized:

Draw and Edit?

Note the different measurements of currents and voltages on the following table

Tableau. 3

| $V''_1$ | $V''_2$ | $V''_3$ | $I''_1$ | $I''_2$ | $I''_3$ |
|---------|---------|---------|---------|---------|---------|
|         |         |         |         |         |         |

### 3.2. Work to be done

- a. What is the equipment used to make these montages?
- b. Theoretically calculate the terminal voltages of the resistors  $R_1$ ,  $R_2$  and  $R_3$  using the superposition theorem.
- c. Theoretically calculate the currents in all branches using the superposition theorem.
- d. From the values of the voltages found previously (practically measuring and calculating theoretically), can we say that the superposition theorem is verified in the case of these voltages? What for?
- e. From the currents found previously (practically measuring and calculating theoretically), can we say that the superposition theorem is verified in the case of currents? What for?
- f. The power dissipated in a resistor is given by the following relationship:  
 $P = I_2^2 R = VI$ . Verified whether or not the superposition theorem can be used to calculate the power dissipated by a resistor ( $R_1$ ,  $R_2$  and  $R_3$ ) (i.e.: is  $P = P' + P''$  or not).