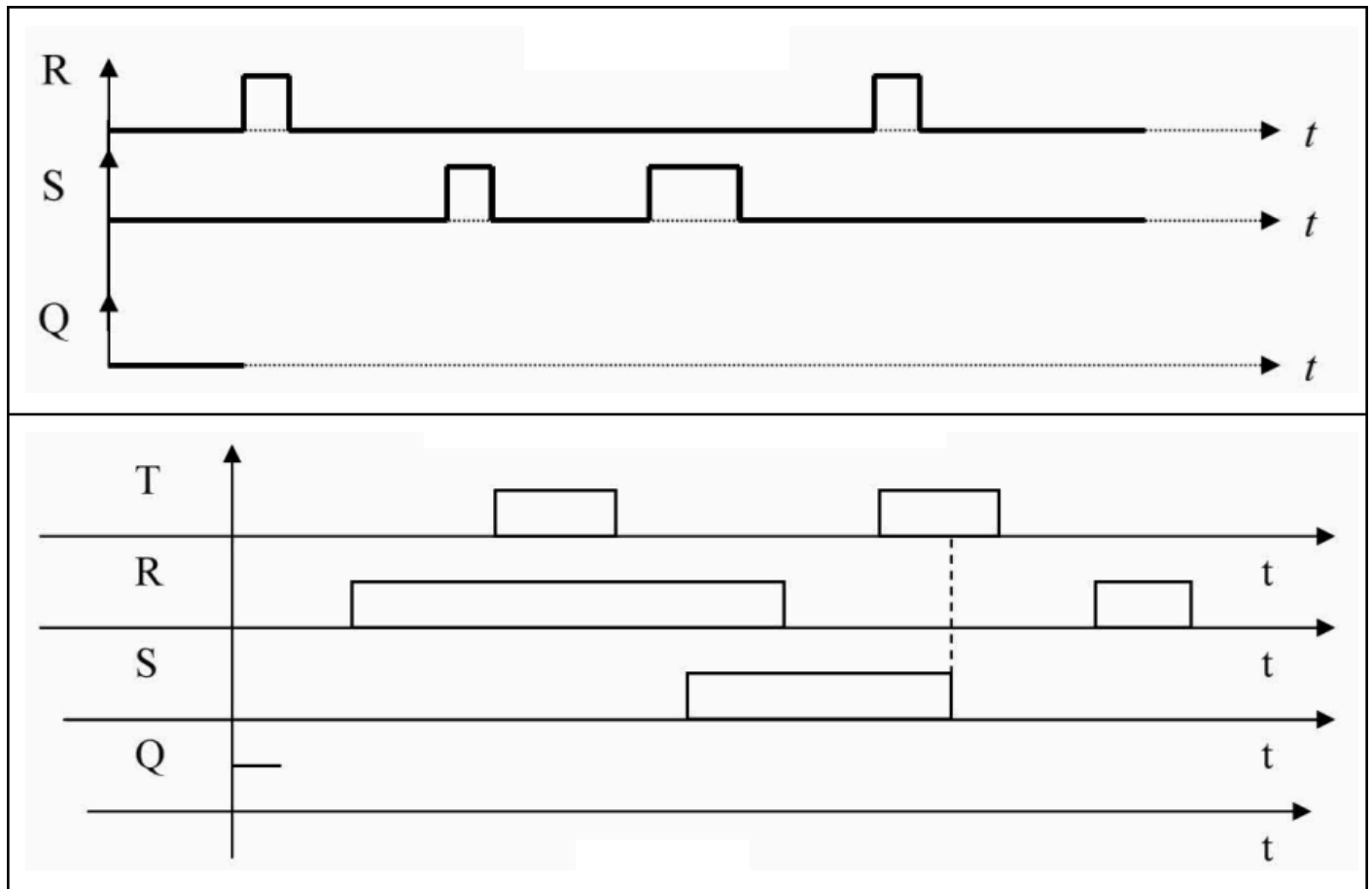


Sequential Logic


Exercise 1:

- 1- Complete the chronogram (timing diagram) of the RS latch.
- 2- Complete the chronogram of the SRT latch synchronized on the high level of T.




Exercise 2:


- 1- Complete the chronogram determining the operation of the D latch for each case where the latch responds to the synchronizations of the designated clock signal.

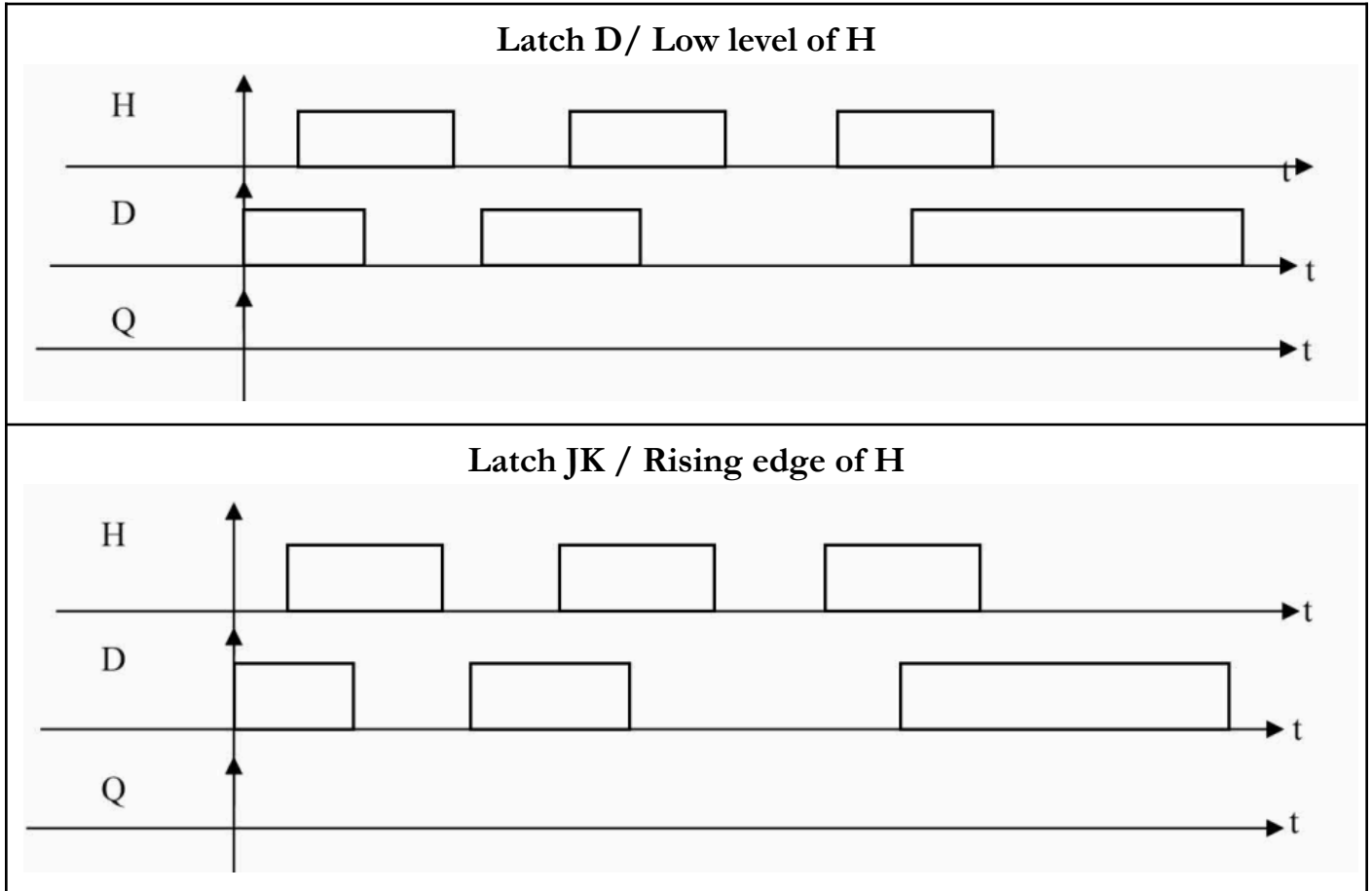

Exercise 3:



Complete the chronogram associated with the synchronized JK latch as follows:

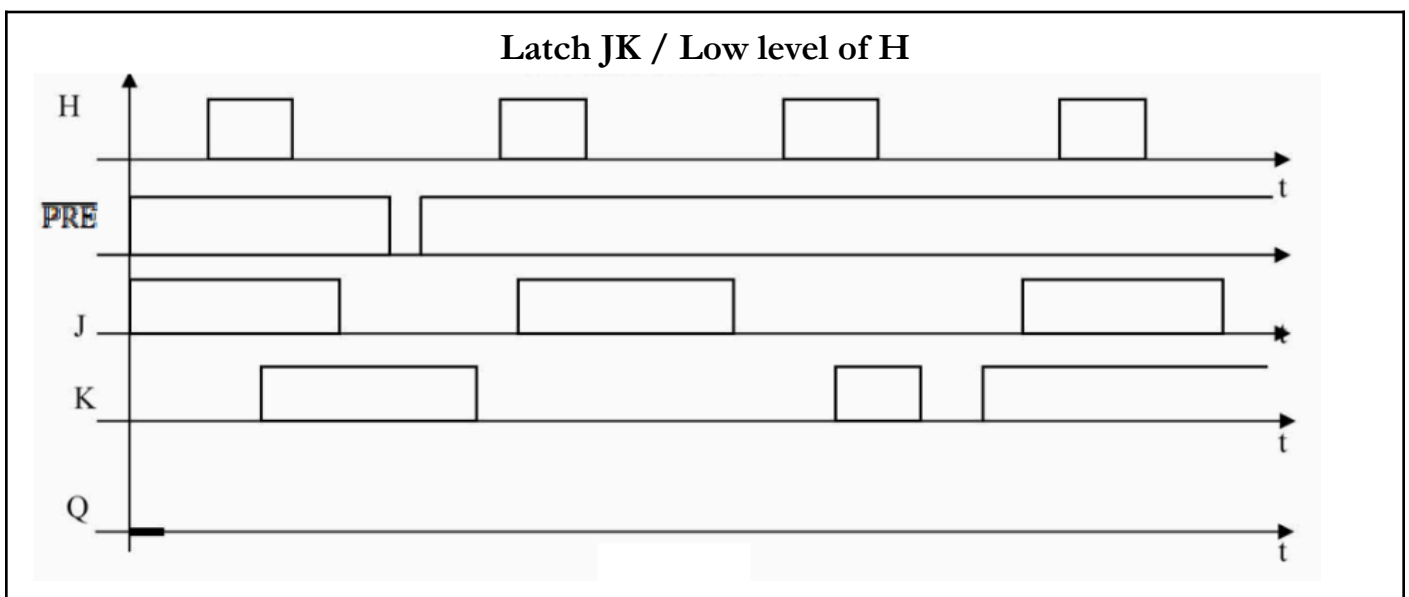

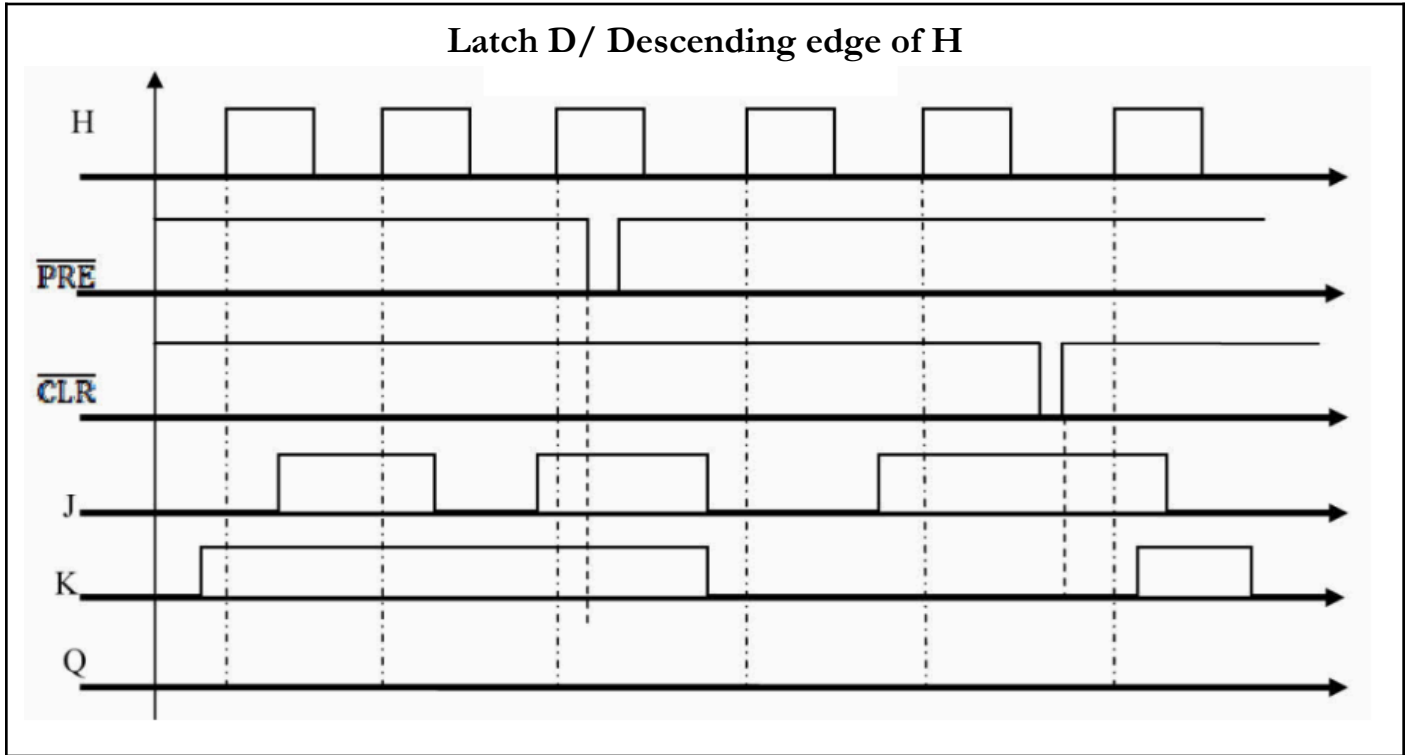



Exercise 4: Consider the circuit shown in the following figure:

- 1- Complete the chronogram associated with this circuit.
- 2- Deduce the role of this circuit.

  

Exercise 5: Consider the circuit shown in the following figure:



- 1- Complete the chronogram associated with this circuit (for each case of E).
- 2- Deduce the role of this circuit (for each case of E).

  

  Exercise 6:


Considering the following implementation:

- 1- Complete the chronogram associated with this circuit and deduce the role of this circuit.





- 2- By slightly modifying the implementation of the previous figure, we obtain the implementation illustrated in the following figure:

 - what does this circuit achieve (justify your answer)




- 3- Considering the following implementation:

  - Complete the chronogram associated with this circuit and deduce the role of this circuit.




- 4- Wire the implementation from the previous figure to achieve an asynchronous modulo-14 counter

 

 Exercise 7:

Considering the following circuit:

1- Complete the chronogram associated with this circuit




2- What is the sequence of output signals obtained? and what is the function performed?

3- Study and give the diagram of a modulo 8 asynchronous counter with D latch?

4- Considering the new circuit:

 - Complete the chronogram associated with this circuit



5- What is the sequence of output signals obtained? and what is the function performed?

6- Study and give the diagram of a modulo 8 asynchronous decrement counter with D latch?