


Series exercises No. 01

Exercise 1 :

1. Write and represent the logical expressions (\bar{A} , $A . B$, $A + B$) using only the expression corresponding to the logic gate:
 - A. "NAND" only.
 - B. "NOR" only.
2. Using the gate "AND", write and represent the next formula: $A.(B + \bar{C})$.

Exercise 2 :

Simplify the following logic circuit who used the logic "Exclusive Not-Or" gate ($A \oplus B = A \odot B$) of manner that the result contains one and only one "Exclusive Not-Or" gate.

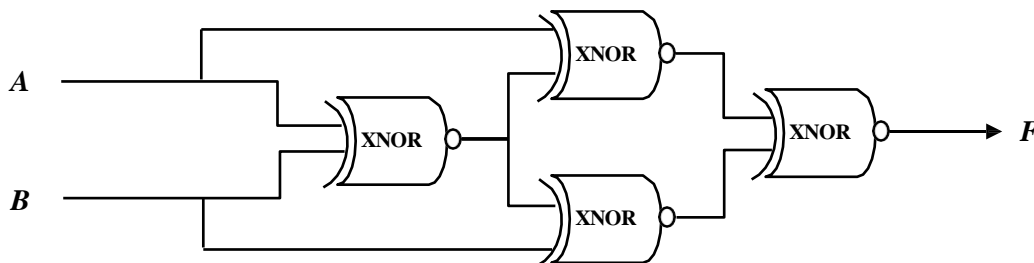

Exercise 3:

Let be three switches which control the operation of two lamps according to the following conditions:

1. The first lamp works only if at least one switch is closed.
2. The second lamp only works if at least two switches are closed.

Questions :

- A. Find the expressions of the logic functions and create the corresponding combinatorial logic circuit.
- B. Write the expressions of the logic functions found in question (A.) using the logic expression corresponding to the "NAND" logic gate only, and then represent the corresponding flowchart.
- C. Write the expressions for the logic functions found in question (A.) using the logic expression corresponding to the "NOR" logic gate only, then represent the corresponding flowchart.