

# Combinatorial logic

## Exercise series 02

### Exercise 1

Make the full adder of a step i using Half Adders.

### Exercise 2

Using a 3 select (address) line multiplexer (MUX), perform the following function:

$$F(A, B, C) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D} + A\bar{B}\bar{C}\bar{D} + AB\bar{C}\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D}$$


### Exercise 3

Consider two 4-bit binary numbers, A( a<sub>3</sub> a<sub>2</sub> a<sub>1</sub> a<sub>0</sub> ) and B(b<sub>3</sub> b<sub>2</sub> b<sub>1</sub> b<sub>0</sub> ).

1. Give the general diagram of the full adder and the half adder which performs the sum between two bits (a<sub>i</sub> and b<sub>i</sub>).
2. Give the general diagram of the circuit which adds the two numbers A and B using full adders only.
3. Give the general diagram of the circuit which adds the two numbers A and B using a half adder and 3 full adders.

### Exercise 4

Consider the following diagram:

 

1. Give the expression Z for this circuit and determine its role.
2. Directly create the circuit which makes the choice between two numbers X and Y such that each of them is represented on 4 bits.

### Exercise 5

1. Give the truth table of the combinatorial circuit which makes the transformation of a number written in a BCD code X(x<sub>3</sub>x<sub>2</sub>x<sub>1</sub>x<sub>0</sub>) to a number written in the 7-segment code (see the figure).
2. Simplify the function corresponding to segment (a) .
3. Represent the circuit corresponding to the simplified function.

