

 


Exercise:

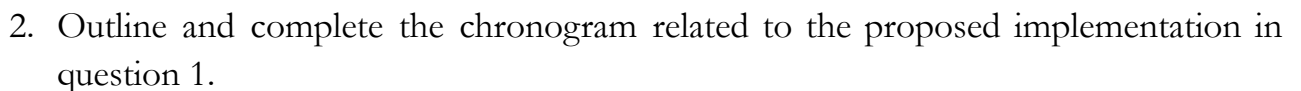1. Propose a symbolic diagram allowing the creation of this counter using 4 latches (Q_A, Q_B, Q_C, Q_D).



Consider the following implementation:

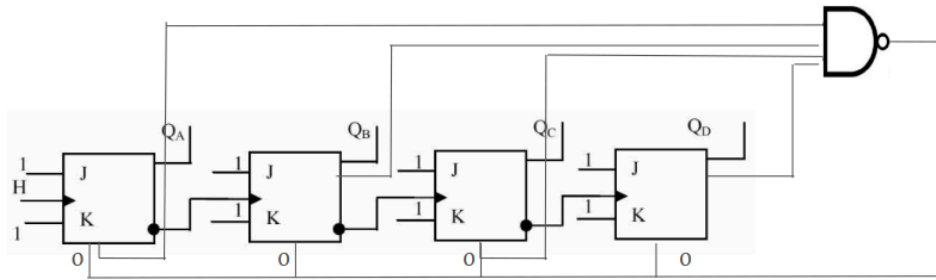

3. Deduce the role of this implementation by justifying the objective of using JK latches.

- This circuit is an asynchronous counter modulo 10. It counts from 0 to 9.
- The objective of using a JK flip-flop is to enable it to be locked in a specific value by forcing both its PRE and CLK inputs to be either 0 or 1.

4. How can we modify this implementation to have an asynchronous down counter module 10.

There are two methods to achieve down counter from a counter:

- By changing the synchronization mode from a rising edge mode to a descending edge mode. (figure 1)
- By modifying the synchronization signal: each latch is synchronized by the resulting signal from the previous latch.

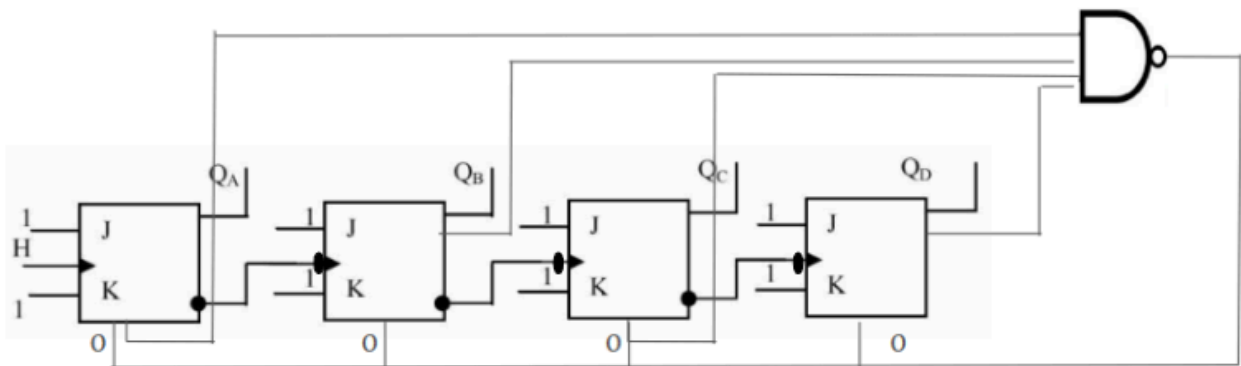


Figure 1

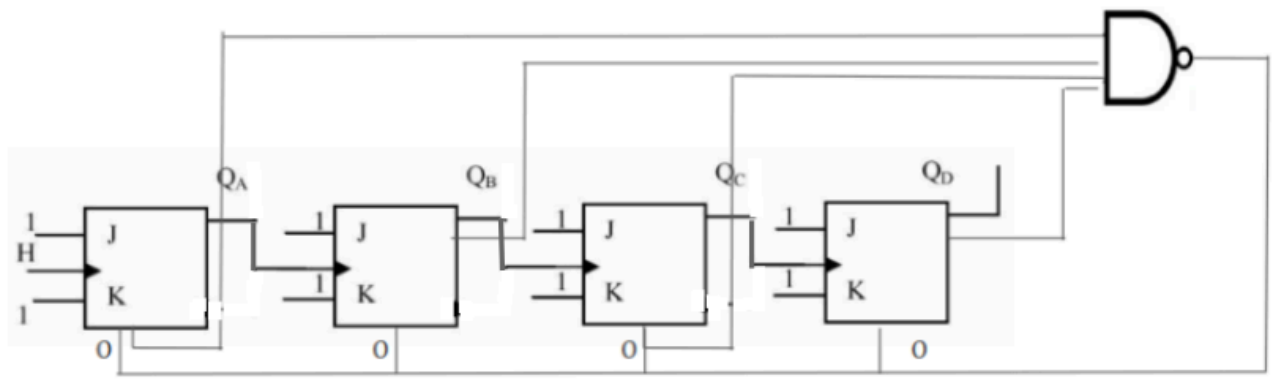


Figure 2