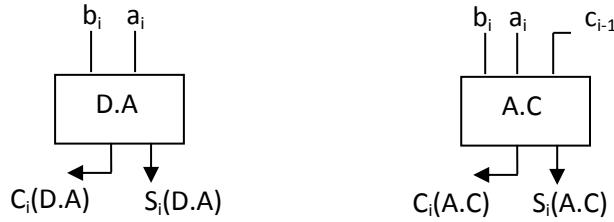


Solution to series 02 exercises

Exercise 1



$$S_i(H.A) = a_i \oplus b_i$$

$$C_i(H.A) = a_i b_i$$

$$S_i(F.A) = a_i \oplus b_i \oplus c_{i-1}$$

$$= S_i(H.A) \oplus c_{i-1} \dots \dots \dots \dots \dots \dots \quad (1)$$


$$C_i(F.A) = \bar{c}_{i-1} a_i b_i + c_{i-1} \bar{a}_i b_i + c_{i-1} a_i \bar{b}_i + c_{i-1} a_i b_i$$

$$= c_{i-1} (a_i \bar{b}_i + \bar{a}_i b_i) + a_i b_i (\bar{c}_{i-1} + c_{i-1})$$

$$= c_{i-1} (a_i \oplus b_i) + a_i b_i (1)$$

$$= c_{i-1} S_i(H.A) + a_i b_i$$

$$= c_{i-1} S_i(H.A) + C_i(H.A) \dots \dots \dots \dots \dots \dots \quad (2)$$

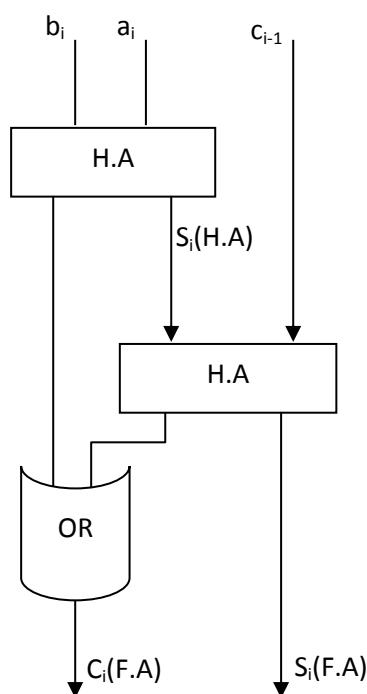

Exercise 2

- We have the formula for the function:

$$F(A, B, C) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}BCD + A\bar{B}CD + AB\bar{C}D + ABC\bar{D} + A\bar{B}\bar{C}\bar{D}$$


- We will find the formula of the MUX with 3 selection lines

The general notation of a multiplexer is as follows: MUX 2^n to 1,
such that n represents the number of selection lines.

We have 3 selection lines, so $n = 3$.

Then the notation will be as follows: MUX 2^3 to 1 \equiv MUX 8 to 1

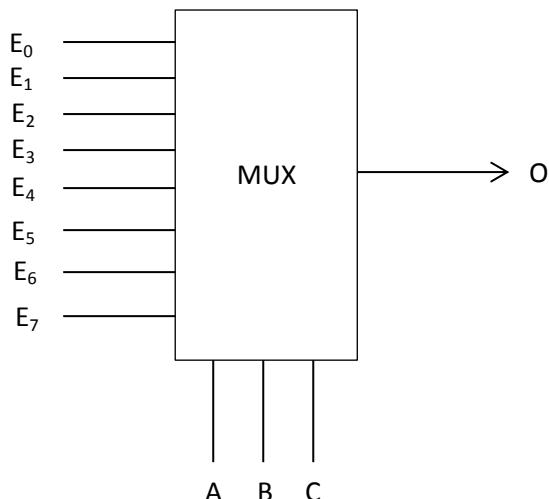Then the number of Entries (Inputs) is 8. The general diagram will be as follows:



The truth table is:

A	B	C	O
0	0	0	E ₀
0	0	1	E ₁
0	1	0	E ₂
0	1	1	E ₃
1	0	0	E ₄
1	0	1	E ₅
1	1	0	E ₆
1	1	1	E ₇

The formula for the MUX output will be as follows:

$$O = \bar{A}\bar{B}\bar{C}E_0 + \bar{A}\bar{B}CE_1 + \bar{A}B\bar{C}E_2 + \bar{A}BCE_3 + A\bar{B}\bar{C}E_4 + A\bar{B}CE_5 + AB\bar{C}E_6 + ABCE_7$$

- We will now compare the two formulas O and F term by term to find the correspondences between the variables.

The two formulas have the three variables A, B, and C in common. The difference lies in the 4th variable. For function F, the variable is D while for Output O, the 4th variable is one of E_i , $i = 0, 1, \dots, 7$.

$$F(A, B, C) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}BCD + A\bar{B}CD + AB\bar{C}D + ABC\bar{D} + A\bar{B}\bar{C}\bar{D}$$


$$= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}CD + AB\bar{C}D + ABC\bar{D}$$

$$O = \bar{A}\bar{B}\bar{C}E_0 + \bar{A}\bar{B}CE_1 + \bar{A}B\bar{C}E_2 + \bar{A}BCE_3 + A\bar{B}\bar{C}E_4 + A\bar{B}CE_5 + AB\bar{C}E_6 + ABCE_7$$

So, by comparing the two formulas we find:

$$\left[E_0 = D, E_1 = \bar{D}, E_2 = \bar{\bar{D}}, E_3 = D, E_4 = \bar{D}, E_5 = D, E_6 = D, E_7 = \bar{D} \right]$$

From where, we represent the function F as follows

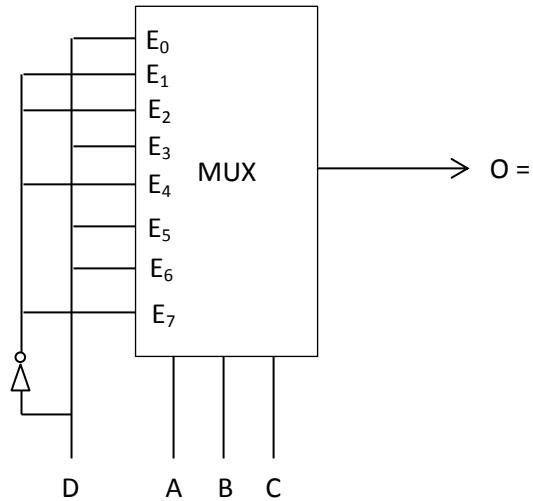


Exercise 3

1. The Full Adder and the Half Adder

1.1. The Full Adder

Truth table:

c_{i-1}	a_i	b_i	S_i	C_i
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

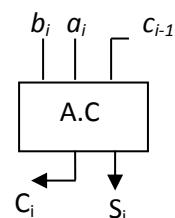

Karnaugh table and Simplification:

C_i	$a_i b_i$	00	01	11	10
c_{i-1}	0	0	0	1	0
	1	0	1	1	1


S_i	$a_i b_i$	00	01	11	10
c_{i-1}	0	0	1	0	1
	1	1	0	1	0

$$C_i = a_i b_i + c_{i-1} a_i + c_{i-1} b_i \quad (*)$$

$$S_i = \overline{c_{i-1}} \bar{a}_i b_i + \overline{c_{i-1}} a_i \bar{b}_i + c_{i-1} \bar{a}_i \bar{b}_i + c_{i-1} a_i b_i \quad (**)$$

$$= a_i \oplus b_i \oplus c_{i-1} \quad (***)$$

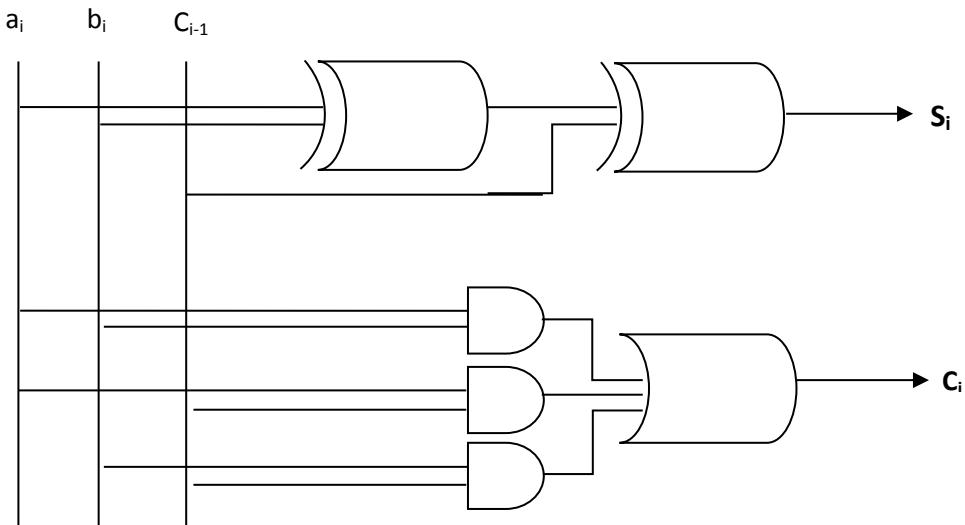
Flowchart: for S_i , the representation could be made by (*) or (**)



1.2. The Half Adder

Truth table:

a_i	b_i	S_i	C_i
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

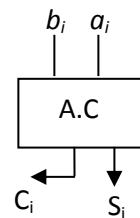


Simplification : directly from the truth table

$$S_i = a_i \bar{b}_i + \bar{a}_i b_i \quad (*)$$


$$= a_i \oplus b_i \quad (**) \quad (***)$$

$$C_i = a_i b_i$$

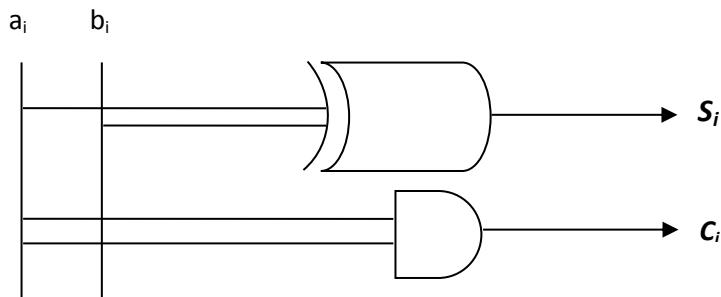
Flowchart: for S_i , the representation could be made by (*) or (**)



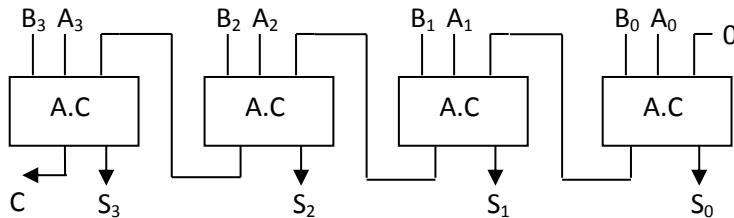2. The adder of A and B using full adders only




3. Adding A and B using a Half Adder and 3 Full Adders

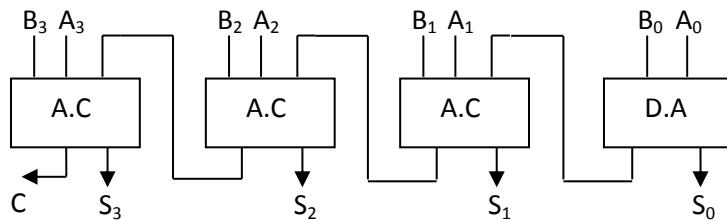

Exercise 4

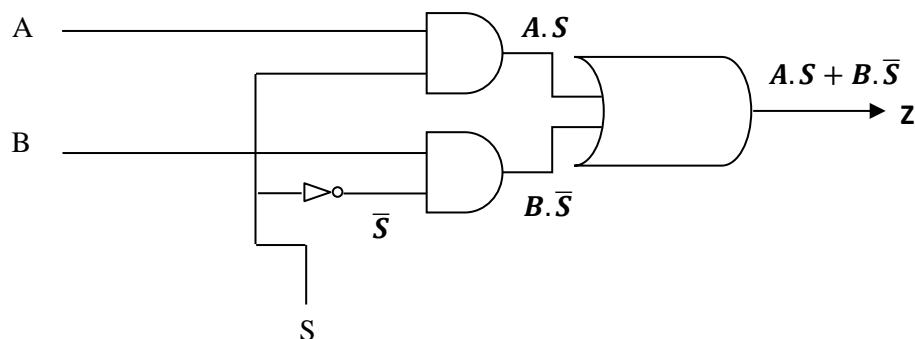1. The expression of Z and the role of the circuit



$$\Rightarrow Z = A \cdot S + B \cdot \bar{S}$$

We will establish the truth table:

S	H_{AS}	B	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

The value of B


The value of A

⇒ The circuit allows one bit to be selected at a time.

⇒ It is a multiplexer: MUX 2 to 1.

2. Direct creation of the circuit

Let be the numbers: $X(X_3 X_2 X_1 X_0)$ and $Y(Y_3 Y_2 Y_1 Y_0) \Rightarrow$ to select the 4 bits of a number, we will use 4 multiplexers: MUX 2 to 1.

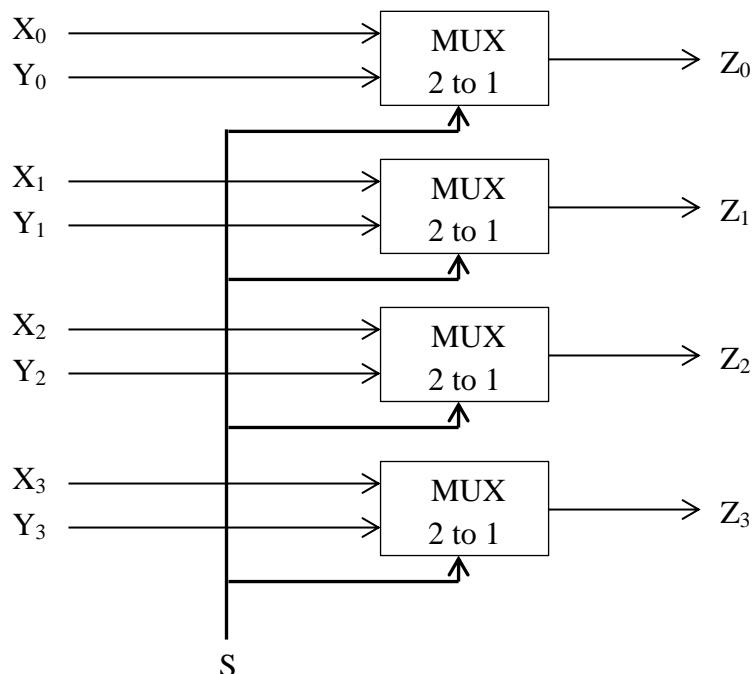


Exercise 5


1. The truth table:

X_3	x_2	X_1	X_0	has	b	vs	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1

0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

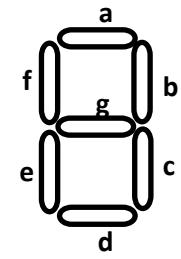

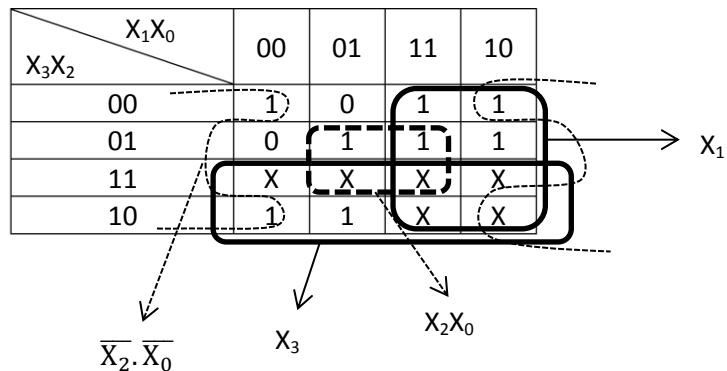2. Simplification of the function corresponding to segment (a)



3. Representation

$$\longrightarrow a = X_1 + X_3 + X_2 \cdot X_0 + \overline{X_2} \cdot \overline{X_0}$$

