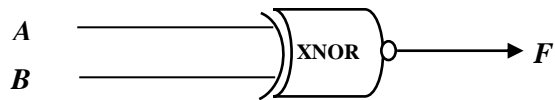


Exercise 2:

$$\begin{aligned}
 F &= (A \odot (A \odot B)) \odot (B \odot (A \odot B)) \\
 &= \overline{\overline{A \oplus (A \oplus B)} \oplus B \oplus (A \oplus B)} \\
 &= \overline{\overline{A \oplus (A.B + \bar{A}.\bar{B})} \oplus B \oplus (A.B + \bar{A}.\bar{B})} \\
 &= \overline{((A.(A.B + \bar{A}.\bar{B}) + \bar{A}.(A.B + \bar{A}.\bar{B})) \oplus (B.(A.B + \bar{A}.\bar{B}) + \bar{B}.(A.B + \bar{A}.\bar{B})))} \\
 &= \overline{((A.(A.B + \bar{A}.\bar{B}) + \bar{A}.(A.\bar{B} + \bar{A}.B)) \oplus (B.(A.B + \bar{A}.\bar{B}) + \bar{B}.(A.\bar{B} + \bar{A}.B)))} \\
 &= \overline{(((A.A.B + A.\bar{A}.\bar{B}) + (\bar{A}.A.\bar{B} + \bar{A}.\bar{A}.B)) \oplus ((B.A.B + B.\bar{A}.\bar{B}) + (\bar{B}.A.\bar{B} + \bar{B}.\bar{A}.B)))} \\
 &= \overline{(((A.B + 0) + (0 + \bar{A}.B)) \oplus ((A.B + 0) + (A.\bar{B} + 0)))} \\
 &= \overline{(A.B + \bar{A}.B) \oplus (A.B + A.\bar{B})} \\
 &= \overline{(B.(A + \bar{A})) \oplus (A.(B + \bar{B}))} \\
 &= \overline{(B.(1)) \oplus (A.(1))} \\
 &= \overline{(B) \oplus (A)} \\
 &= \overline{A \oplus B} \\
 &= A \odot B
 \end{aligned}$$



Exercise 3:

A. Normal expressions and representations (without NAND and NOR)

1) Determination of input and output variables:

- We have 03 input variables representing the 03 switches which are represented by A, B, and C respectively.
- We have 02 output variables representing the 02 lamps which are represented by L1 and L2 respectively.

2) Truth table:

- **Variables:** I1, I2 and I3 binary (boolean) variables → **1** closed switch,
→ **0** open switches.
- **Functions:** L1 and L2 binary functions (boolean) → **1** lamp works,
→ **0** lamp does not work.

I1	I2	I3	L1	L2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1


1) **Simplification:**

L1					
I2 I3 \ I1	00	01	11	10	
0	0	1	1	1	
1	1	1	1	1	

L2					
I2 I3 \ I1	00	01	11	10	
0	0	0	1	0	
1	1	0	1	1	


$$L1(I1, I2, I3) = I1 + I2 + I3 \quad L2(I1, I2, I3) = I1.I2 + I1.I3 + I2.I3$$

2) **Flowcharts:**

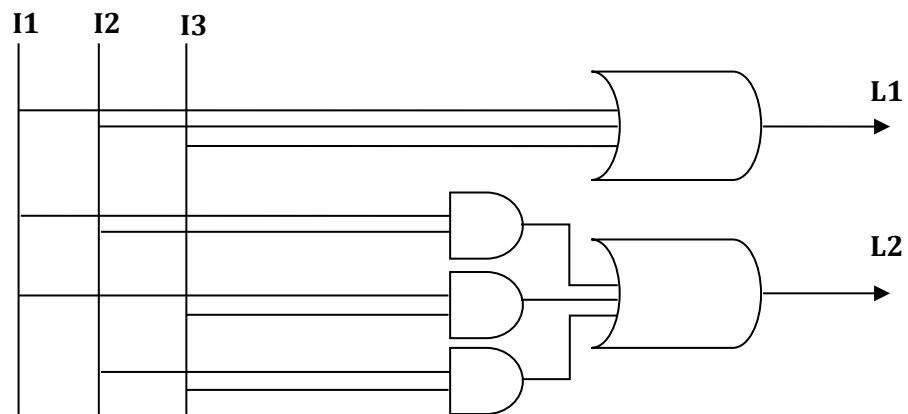


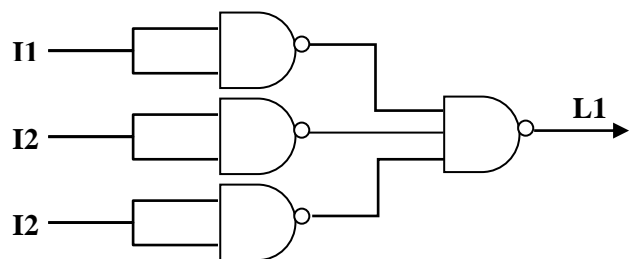B. **Expressions and representations with NAND**

$$\begin{aligned} L1(I1, I2, I3) &= I1 + I2 + I3 \\ &= \overline{\overline{I1 + I2 + I3}} \\ &= \overline{\overline{I1} \cdot \overline{I2} \cdot \overline{I3}} \\ &= \overline{\overline{I1} \cdot \overline{I2} \cdot \overline{I3}} \end{aligned}$$



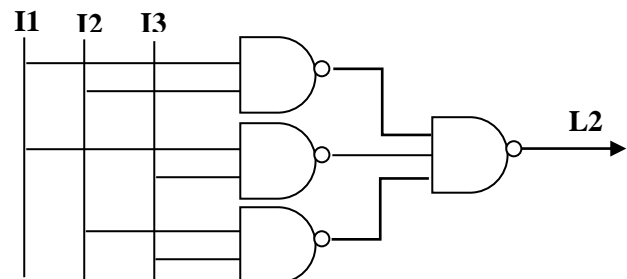
$$\begin{aligned} L2(I1, I2, I3) &= I1.I2 + I1.I3 + I2.I3 \\ &= \overline{\overline{I1.I2 + I1.I3 + I2.I3}} \\ &= \overline{\overline{I1.I2} \cdot \overline{I1.I3} \cdot \overline{I2.I3}} \end{aligned}$$



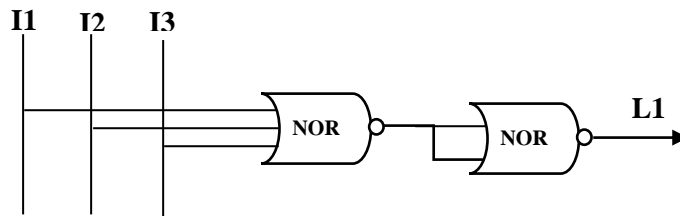C. Expressions and representations with NOR

$$\begin{aligned}
 L1(I1, I2, I3) &= I1 + I2 + I3 \\
 &= \overline{\overline{I1 + I2 + I3}} \\
 &= \overline{\overline{I1 + I2 + I3} + \overline{I1 + I2 + I3}}
 \end{aligned}$$



$$\begin{aligned}
 L2(I1, I2, I3) &= I1.I2 + I1.I3 + I2.I3 \\
 &= \overline{\overline{I1.I2 + I1.I3 + I2.I3}} \\
 &= \overline{\overline{I1.I2} + \overline{I1.I3} + \overline{I2.I3}} \\
 &= \overline{\overline{I1 + I2} + \overline{I1 + I3} + \overline{I2 + I3}} \\
 &= \overline{\overline{I1 + I1 + I2 + I2} + \overline{I1 + I1 + I3 + I3} + \overline{I2 + I2 + I3 + I3}} \\
 &= \overline{\overline{I1 + I1 + I2 + I2} + \overline{I1 + I1 + I3 + I3} + \overline{I2 + I2 + I3 + I3}}
 \end{aligned}$$

